



B.Tech. II Year I Semester Examinations NOVEMBER-2019

SUBJECT: Electronic Device & Circuits

BRANCH : ECE,CSE&IT

Time: 3 Hours

Max. Marks:75

Note: This question paper contains two Parts A and B.

Part A is compulsory which carries 25 Marks. Answer all the questions.

Part B consists of 5 questions. Answer all the questions.

Bloom's Level:

Remember	L1	Analyze	L4
Understand	L2	Evaluate	L5
Apply	L3	Create	L6

PART - A		Bloom's Level	25Marks
ANSWER ALL THE QUESTIONS			
1	Define Static and Dynamic Resistance of P-N diode?	L1	2M
2	What is clipper? Draw the circuit diagram of positive clipper.	L2	3M
3	In a BJT, the emitter current is 12mA and the emitter current is 1.02 times the collector current. Find the base current.	L5	2M
4	Give the h_{ie} and h_{oe} equations of BJT?	L3	3M
5	Explain how transistor acts as an amplifier?	L6	2M
6	Define stability factor of an amplifier. What is ideal value?	L1	3M
7	What is pinch off voltage?	L2	2M
8	Why thermal runaway is not there in FETs?	L4	3M
9	Sketch the ohmic region in drain characteristics of JFET?	L6	2M
10	Why UJT is called as negative resistance device?	L3	3M
PART - B		Bloom's Level	50Marks
ANSWER ALL THE QUESTIONS			
11.i.a)	Explain V-I characteristics of a PN junction diode.	L2	5M
b)	Calculate the factor by which the reverse saturation current in Silicon diode is multiplied when the temperature is increased from 25°C to 70°C.	L5	5M
[OR]			
ii.a)	Explain the operation of Full Wave Rectifier with necessary diagrams.	L3	5M
b)	With a neat circuit diagram and waveforms explain the operation of positive clamper and negative clamper.	L4	5M
12.i.a)	Explain CE configuration with the help of input and output characteristics.	L2	5M
b)	Derive the CC h-parameters in terms of CE h-parameters.	L5	5M
[OR]			
ii.a)	Derive an expression for voltage gain, current gain of CE amplifier using h-parameter model.	L4	5M
b)	Compare CB, CC and CE configurations?	L1	5M
13.i.a)	Derive the expression for the stability factor for self-bias configuration.	L4	5M
b)	Draw the circuit diagram of CB amplifier and derive the expression for voltage gain, input impedance and current gain.	L3	5M
[OR]			
ii.a)	What is biasing? Explain the need of it. List out different types of biasing methods	L2	5M
b)	In a Silicon transistor circuit with a fixed bias, $V_{CC}=9V$, $R_C=3K\Omega$, $R_B=8K\Omega$, $\beta=50$, $V_{BE}=0.7V$. Find the operating point and Stability factor.	L4	5M
14.i.a)	Why we call FET as a Voltage Controlled Device.	L2	5M
b)	Give the comparison between BJT and JFET.	L5	5M
[OR]			
ii.a)	Explain how JFET act as voltage variable resistor.	L4	5M
b)	Explain the working of a depletion type MOSFET with a neat construction diagram and its characteristics.	L2	5M
15.i.	Draw the circuit of source follower amplifier and derive the expressions for A_i , A_v , R_i and R_o .	L4	10M
[OR]			
ii.a)	Explain tunnel diode operation with the help of energy band diagrams.	L1	5M
b)	Explain the static characteristics of SCR.	L2	5M

VJIT(A)